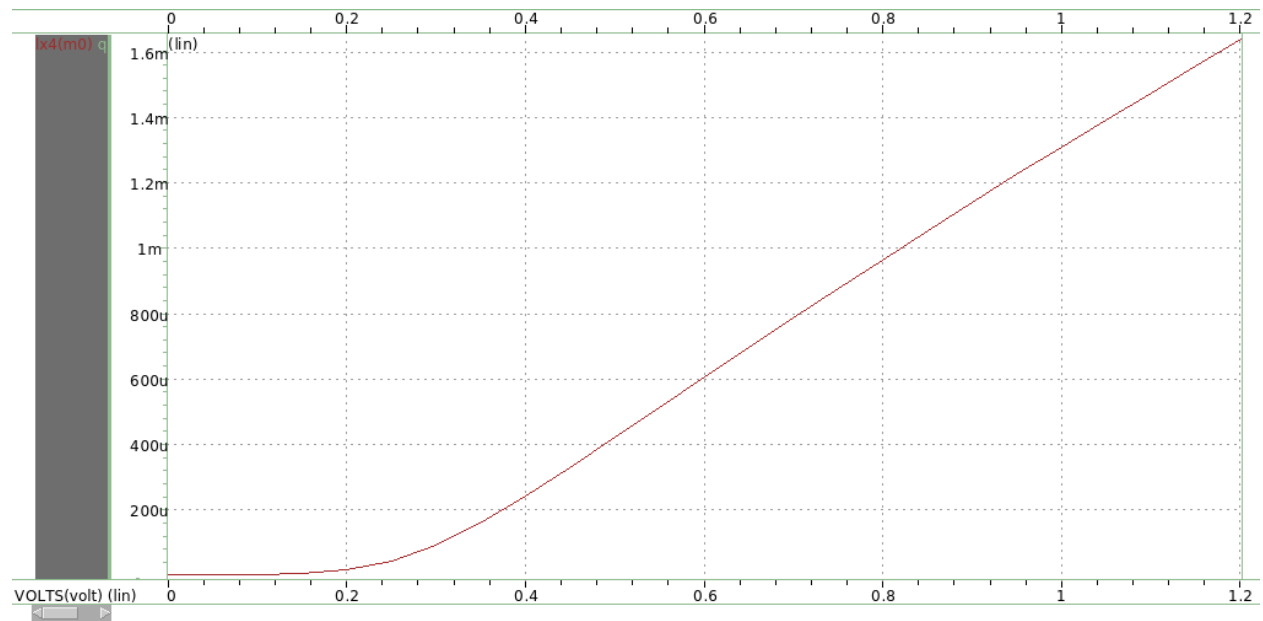


## Q1A



## Q1B

From Q1A, the  $V_{th}$  voltage is approximated at 0.2V.

Figure 2.1: the transistor operates in the linear and saturation region. Saturation occurs at

$$V_{DS} \geq V_{GS} - V_{th} = 0.6 - 0.2 = 0.4$$



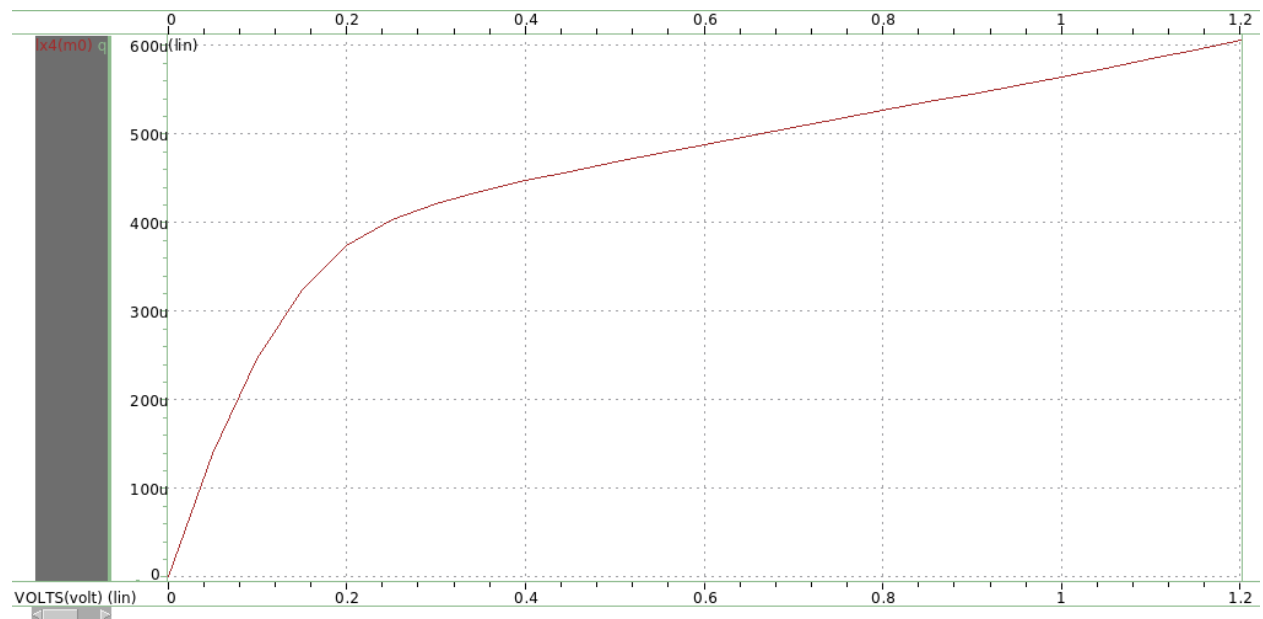


Figure 2.2: the transistor operates in the linear and saturation region. It enters saturation when
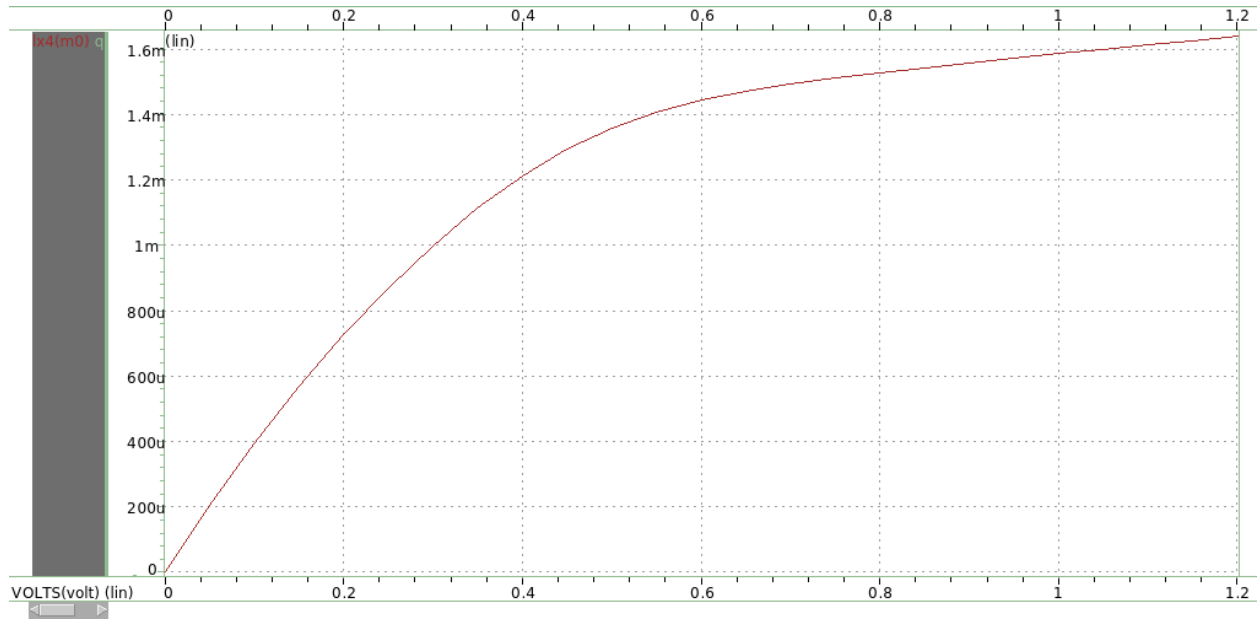
$$V_{DS} \geq V_{GS} - V_{th} = 1.2 - 0.2 = 1.0V$$



Q1C

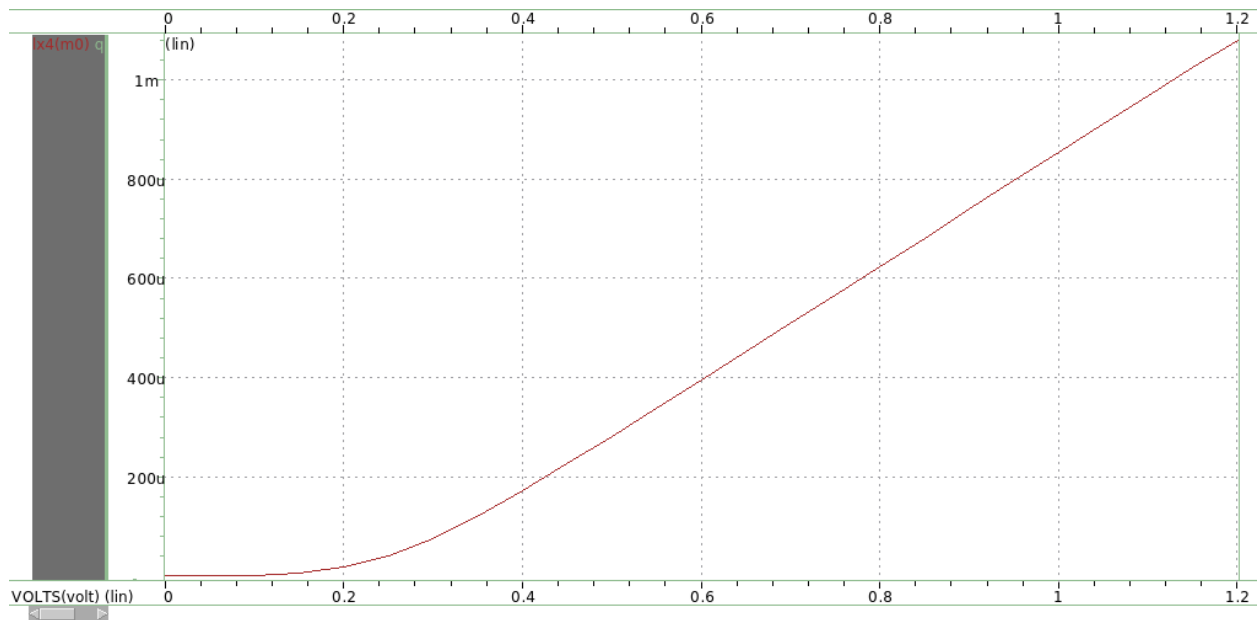

Q1D

Q2A

Figure 5.1



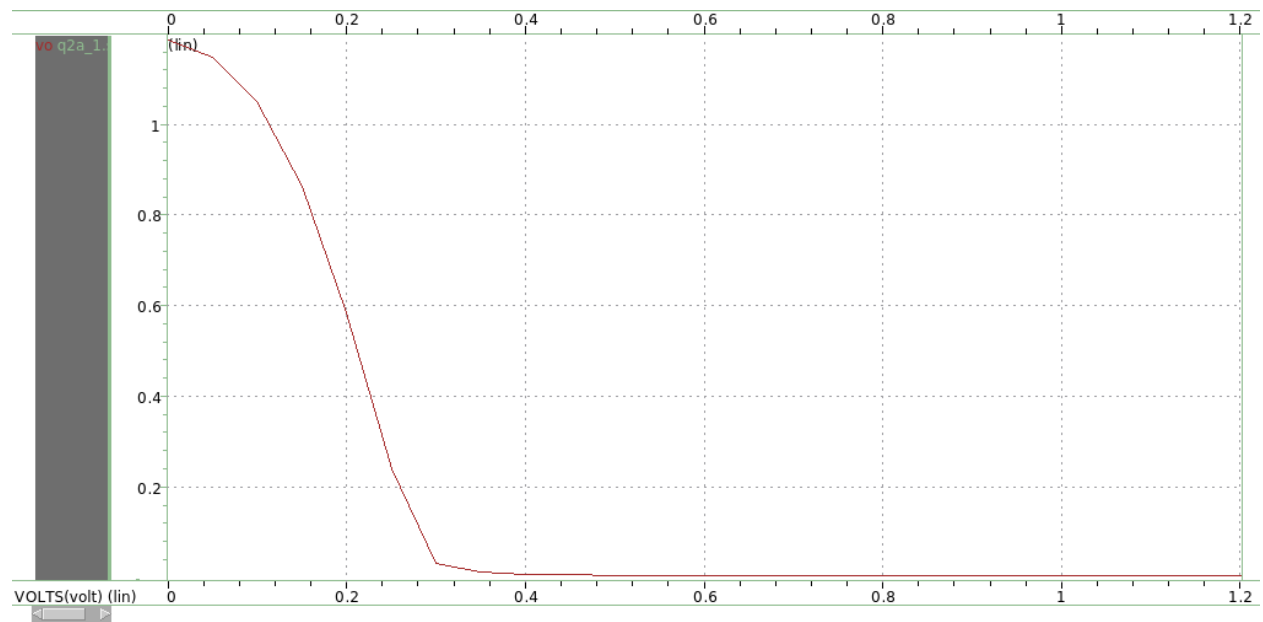


Figure 5.2

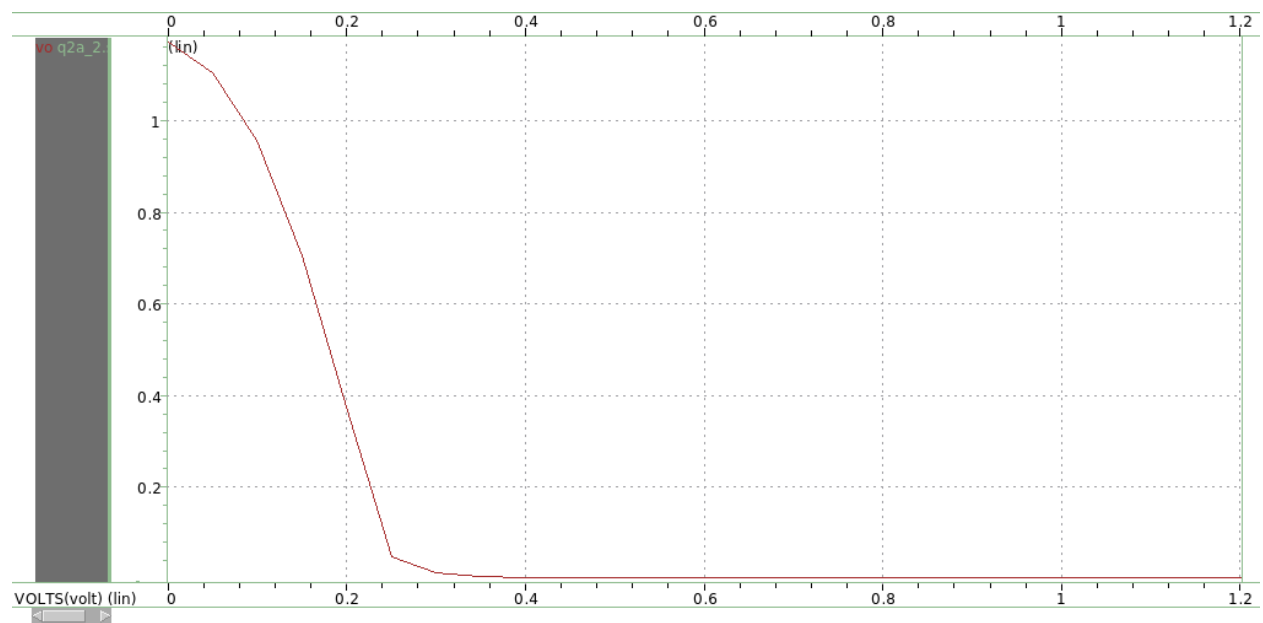


## Q2B


**R0=100K**

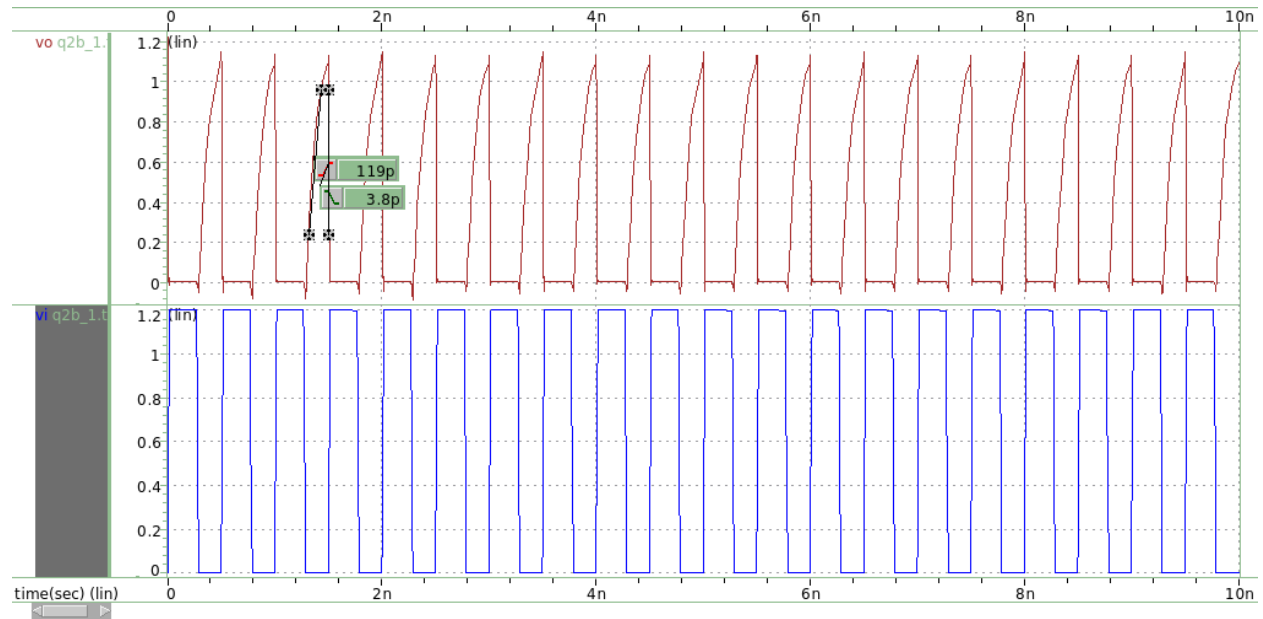


**R0=200K**

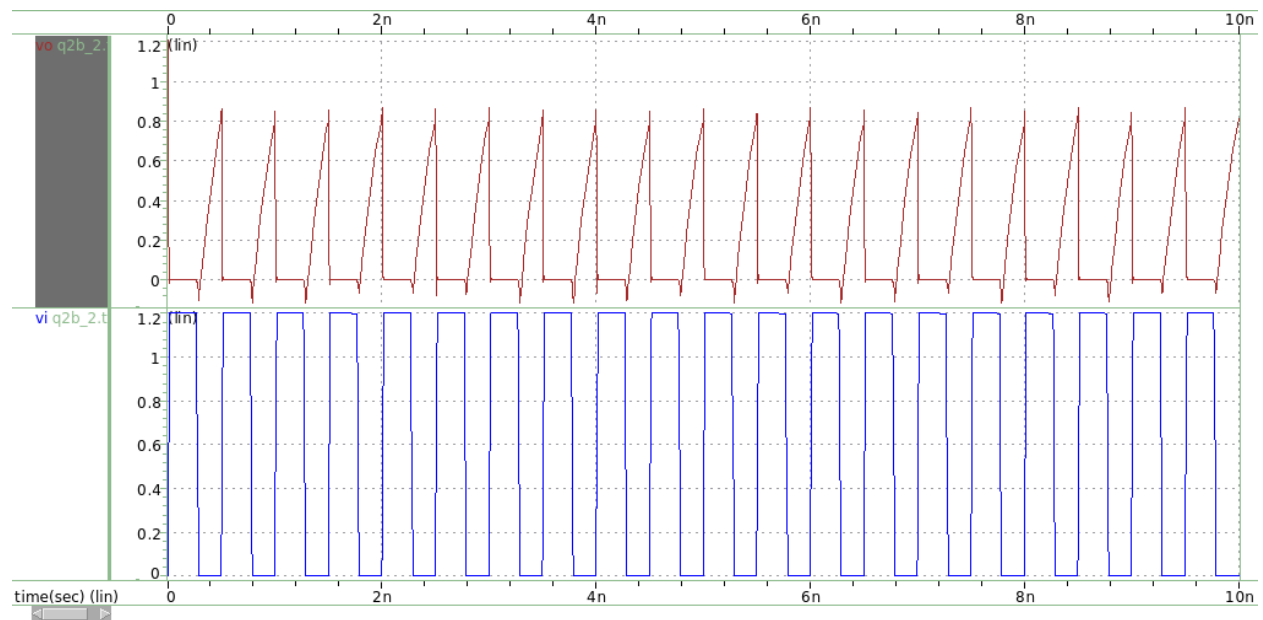

Q3

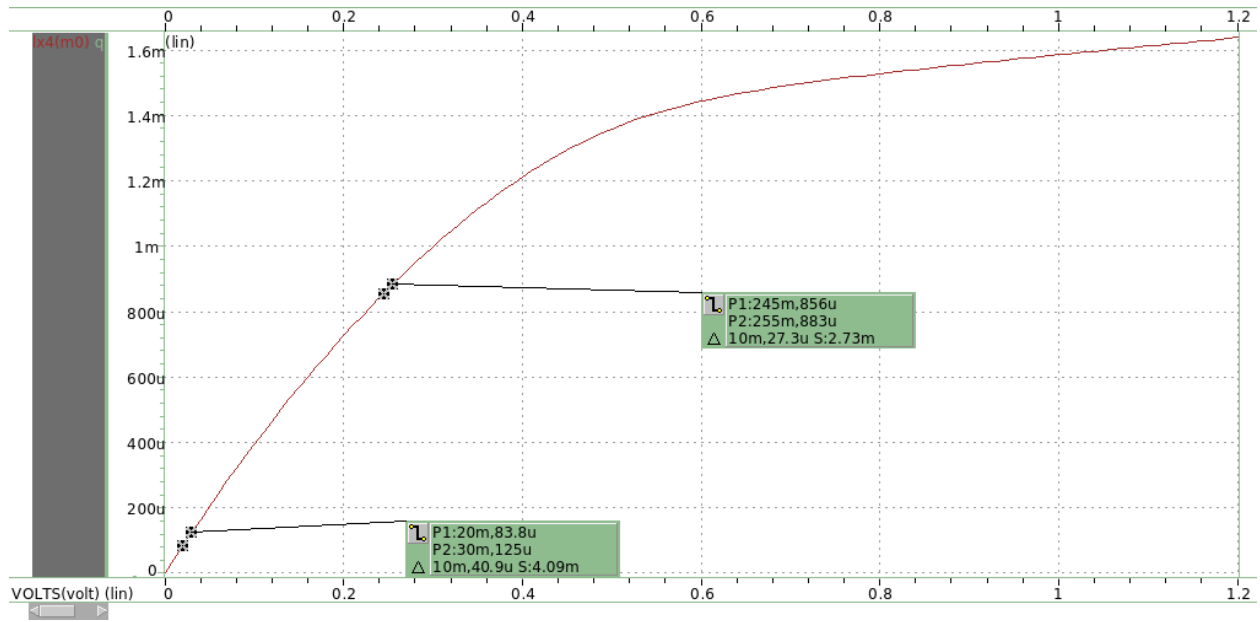

Q4

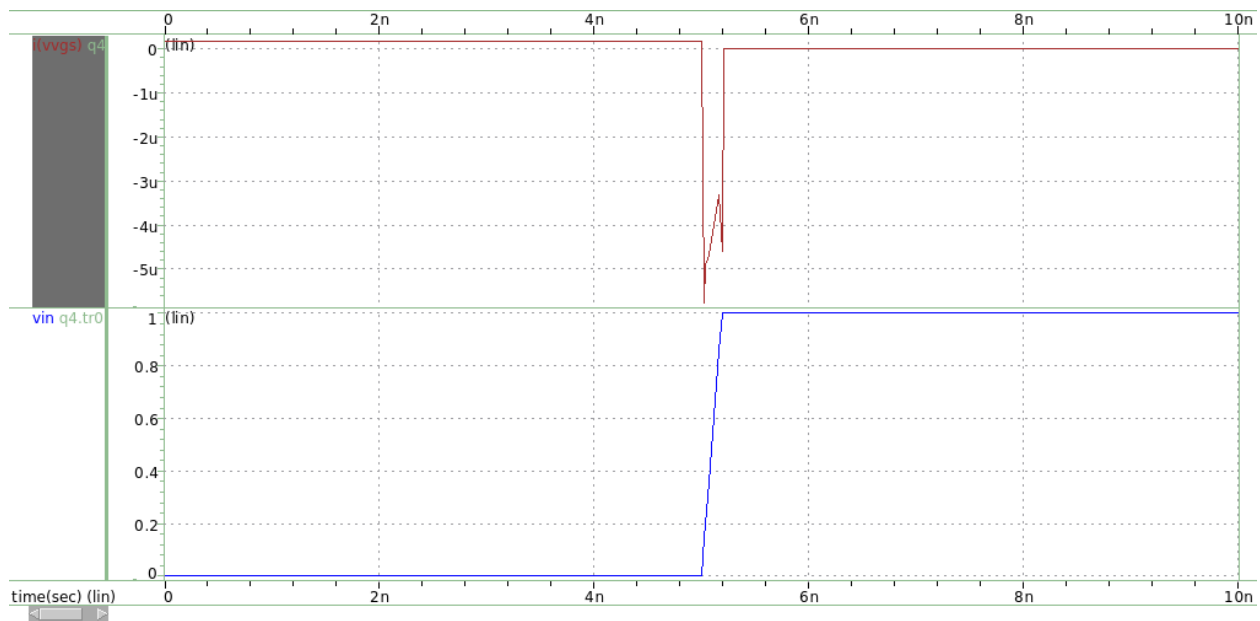

Q5

A

Given,  $V_{th} = 0.2$  from graphical inspection then we can solve a system of equations for  $\beta$  and  $n$ .

$$I = 0.5\beta(V_{GS} - V_{th})^n$$

$$421E - 6 = 0.5\beta(0.5 - 0.2)^n$$

$$965E - 6 = 0.5\beta(0.8 - 0.2)^n$$

Then  $\beta = 0.00356$  and  $n = 1.197$

B

Given,  $V_{th} = 0.2$  from graphical inspection then we can solve a system of equations for  $\beta$  and  $n$ .

$$I = 0.5\beta(V_{GS} - V_{th})^n$$

$$282E - 6 = 0.5\beta(0.5 - 0.2)^n$$

$$624E - 6 = 0.5\beta(0.8 - 0.2)^n$$

Then  $\beta = 0.00224$  and  $n = 1.146$

C

$$\frac{\beta_N}{\beta_P} = \frac{0.00356}{0.00224} = 1.59$$

D